

EE 2240
Problem #03

Determine the equivalent capacitance.

