

EE 2240
Problem #06

The voltage across a $10\ \mu\text{F}$ capacitor is shown. Determine and accurately sketch the current waveform.

