

EE 2240
Problem #11

Given three capacitors with values $2\ \mu\text{F}$, $4\ \mu\text{F}$ and $6\ \mu\text{F}$, can the capacitors be interconnected so that the combination is an equivalent $3\ \mu\text{F}$?