

EE 2240  
**Problem #04**

Use PSpice to determine  $V_x$ .

