

EE 2240  
Problem #07

Use PSpice to determine  $V_x$  and  $I_y$ .

