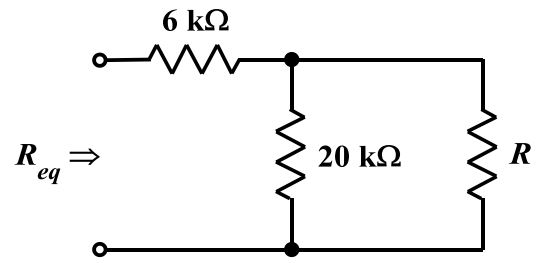


EE 2240  
Problem #01



- Find  $R_{eq}$  if  $R = 5\text{ k}\Omega$ .
- Find  $R_{eq}$  if  $R = 380\text{ k}\Omega$ .
- What value of  $R$  would result in  $R_{eq} = 21\text{ k}\Omega$ ?