

EE 2240  
**Problem #05**

The waveform for the voltage across a 20 mH inductor is shown. Determine, and accurately sketch, the waveform for the inductor current if  $v(t) = 0$  for  $t < 0$ .

