

EE 2240
Problem #07

Find the value of L so that the equivalent inductance will be 2 mH.

