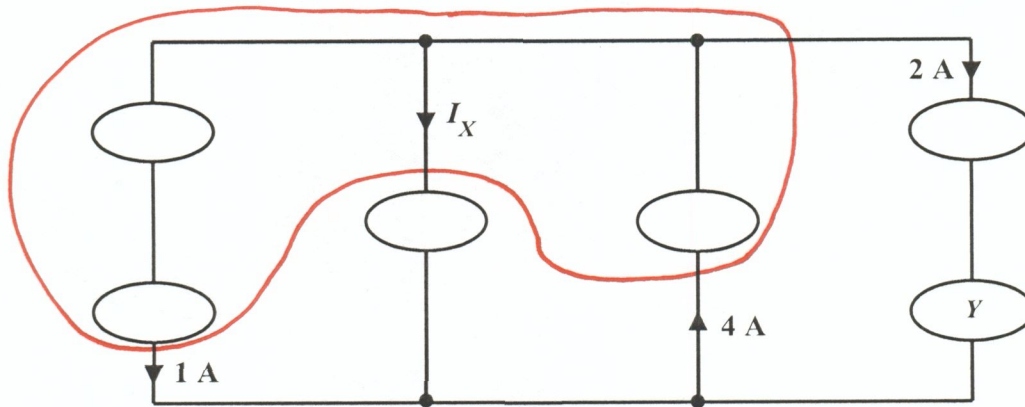


EE 2240
Problem #01

Determine the numerical value of I_x .



$$\text{KCL: } 1A + I_x - 4A + 2A = 0$$

$$\Rightarrow I_x = 1A$$