

EE 2240  
Problem #06

Given  $I_1 = -1 \text{ mA}$ ,  $I_3 = 0.5 \text{ mA}$ , and  $I_6 = 0.2 \text{ mA}$ , find  $I_2$ ,  $I_4$  and  $I_5$ .

