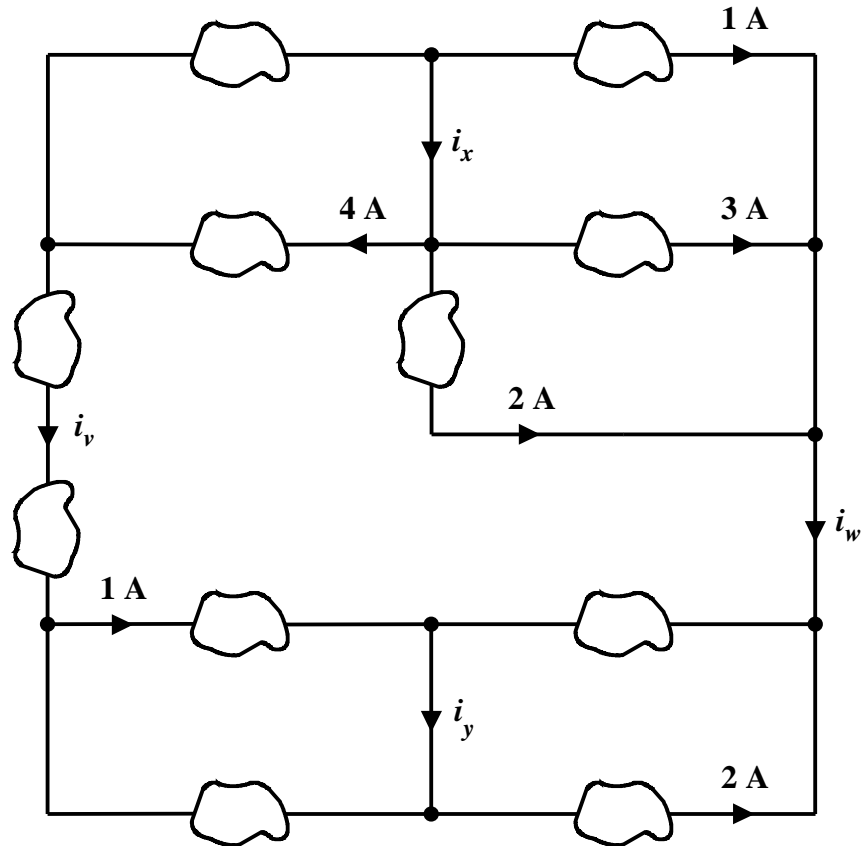


EE 2240
Problem #08

Given the following circuit:



a. Find i_v .

b. Find i_w .

c. Find i_x .

d. Find i_y .