

EE 2240
Problem #11

Find I_1 , I_2 and I_3 .

