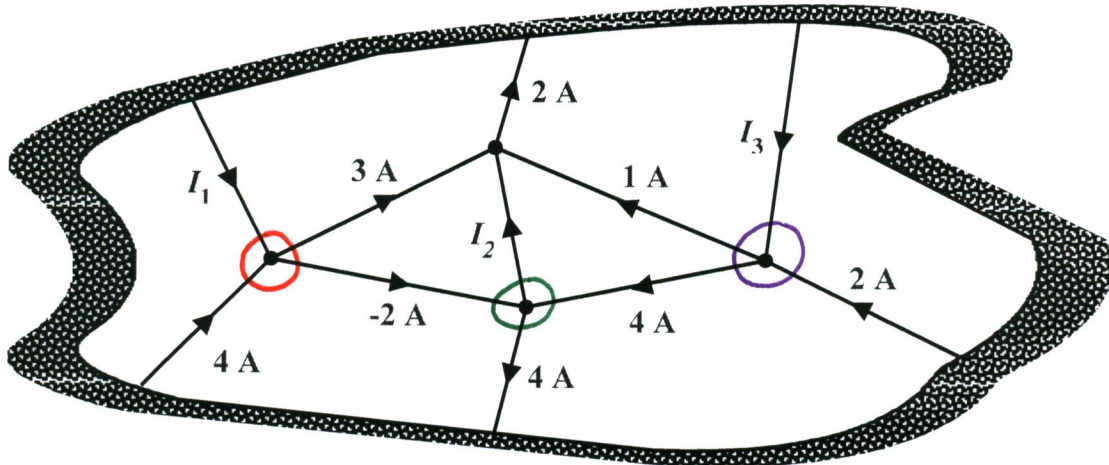


EE 2240
Problem #11

Find I_1 , I_2 and I_3 .



$$I_1 + 4A - (-2A) - 3A = 0$$

$$\Rightarrow I_1 = -3A$$

$$-I_2 + (-2A) - 4A + 4A = 0$$

$$\Rightarrow I_2 = -2A$$

$$I_3 - 1A - 4A + 2A = 0$$

$$\Rightarrow I_3 = 3A$$