

EE 2240
Problem #01

Determine the numerical value of V_Y .

