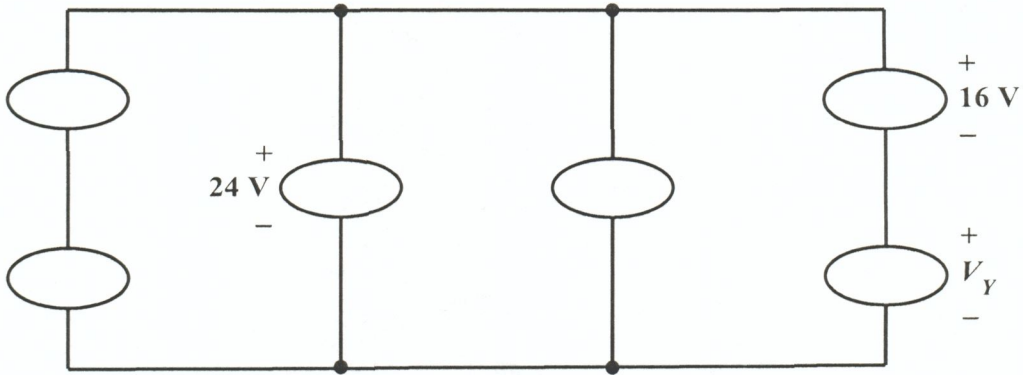


EE 2240
Problem #01

Determine the numerical value of V_y .



$$\text{KVL: } -24\text{V} + 16\text{V} + V_y = 0$$

$$\Rightarrow V_y = 8\text{V}$$