

EE 2240
Problem #02

Determine the numerical value of V_Y .

