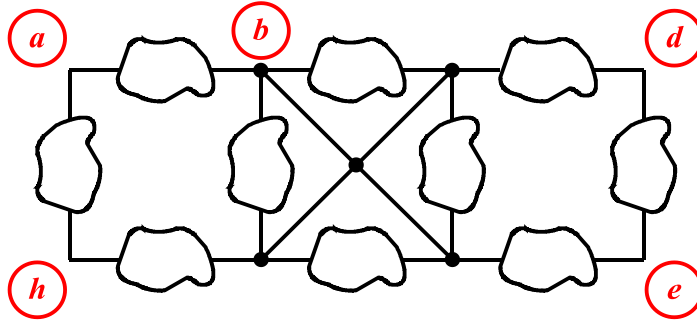


EE 2240
Problem #05



If $V_{ab} = 10 \text{ V}$, $V_{ad} = 12 \text{ V}$, $V_{ah} = 1 \text{ V}$ and $V_{eb} = 3 \text{ V}$:

a. Determine V_{ae} .

b. Determine V_{bd} .

c. Determine V_{be} .

d. Determine V_{dh} .

e. Determine V_{he} .