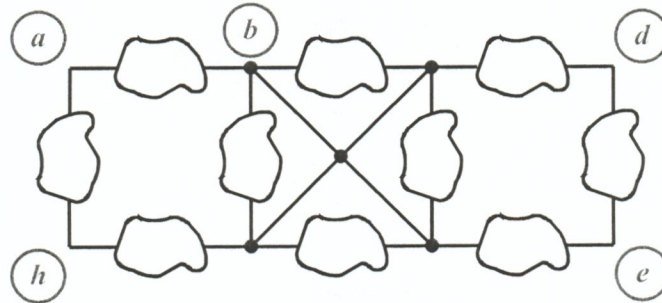


EE 2240
Problem #05



If $V_{ab} = 10\text{ V}$, $V_{ad} = 12\text{ V}$, $V_{ah} = 1\text{ V}$ and $V_{eb} = 3\text{ V}$:

a. Determine V_{ae} .

$$V_{ae} = V_{ab} + V_{be} = V_{ab} - V_{eb} = 10\text{ V} - 3\text{ V} = 7\text{ V}$$

b. Determine V_{bd} .

$$V_{bd} = V_{ba} + V_{ad} = -V_{ab} + V_{ad} = -10\text{ V} + 12\text{ V} = 2\text{ V}$$

c. Determine V_{be} .

$$V_{be} = -V_{eb} = -3\text{ V}$$

d. Determine V_{dh} .

$$V_{dh} = V_{da} + V_{ah} = -V_{ad} + V_{ah} = -12\text{ V} + 1\text{ V} = -11\text{ V}$$

e. Determine V_{he} .

$$\begin{aligned} V_{he} &= V_{ha} + V_{ab} + V_{be} \\ &= -V_{ah} + V_{ab} - V_{eb} \\ &= -1\text{ V} + 10\text{ V} - 3\text{ V} \\ &= 6\text{ V} \end{aligned}$$