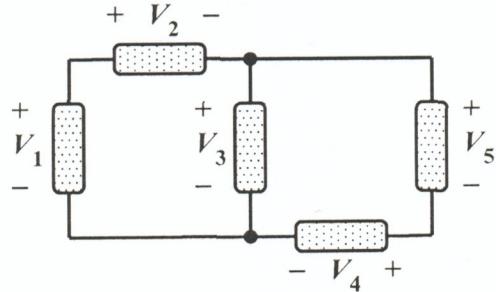


EE 2240
Problem #07

Given $V_2 = 10\text{ V}$, $V_3 = 10\text{ V}$, and $V_4 = 10\text{ V}$, find V_1 and V_5 .



$$\begin{aligned}V_1 &= V_2 + V_3 \\&= 10\text{V} + 10\text{V} \\&= 20\text{V}\end{aligned}$$

$$\begin{aligned}V_5 &= V_3 - V_4 \\&= 10\text{V} - 10\text{V} \\&= 0\text{V}\end{aligned}$$