

EE 2240  
**Problem #10**

Six of the 11 branch voltages have been predetermined. Find the values of the other five:  $V_1$ ,  $V_2$ ,  $V_3$ ,  $V_4$ , and  $V_5$ .

