

EE 2240
Problem #02

Find I_o using linearity and proportionality, and the assumption that $I_o = 1$ mA. Show the details of your work.

