

EE 2240
Problem #03

Use linearity and proportionality to determine V_x . Show all details of your work.

