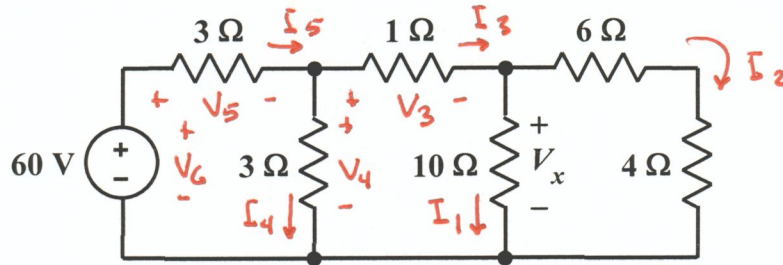


EE 2240
Problem #03

Use linearity and proportionality to determine V_x . Show all details of your work.



Assume $V_x = 10V$ (Any guess is OK.)

$$\text{Then } I_1 = \frac{V_x}{10\Omega} = 1A$$

$$I_2 = \frac{V_x}{6\Omega + 4\Omega} = 1A$$

$$I_3 = I_1 + I_2 = 2A$$

$$V_3 = (1\Omega) I_3 = 2V$$

$$V_4 = V_3 + V_x = 12V$$

$$I_4 = \frac{V_4}{3\Omega} = 4A$$

$$I_5 = I_3 + I_4 = 6A$$

$$V_5 = (3\Omega) I_5 = 18V$$

$$V_6 = V_5 + V_4 = 30V$$

$$\frac{V_x}{60V} = \frac{10V}{V_6} \Rightarrow V_x = 20V$$