

EE 2240  
**Problem #04**

Find  $V_o$  using linearity and proportionality, with the assumption that  $V_o = 4$  V. Show all details of your work.

