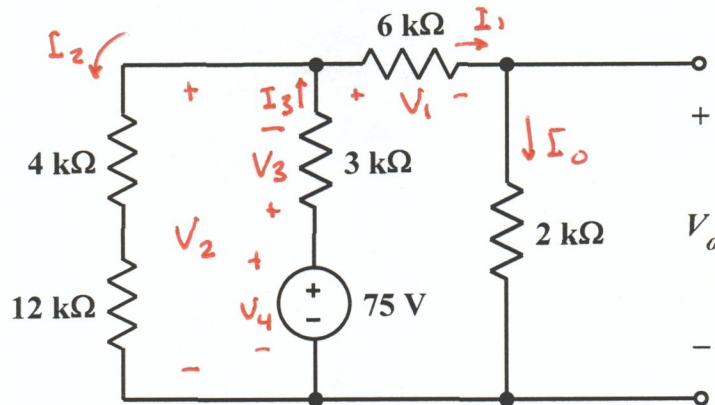


EE 2240
Problem #04

Find V_o using linearity and proportionality, with the assumption that $V_o = 4\text{ V}$. Show all details of your work.



Assume $V_o = 4\text{ V}$.

$$\text{Then } I_0 = \frac{V_o}{2\text{ k}\Omega} = 2\text{ mA}$$

$$I_1 = I_0 = 2\text{ mA}$$

$$V_1 = (6\text{ k}\Omega) I_1 = 12\text{ V}$$

$$V_2 = V_1 + V_o = 16\text{ V}$$

$$I_2 = \frac{V_2}{4\text{ k}\Omega + 12\text{ k}\Omega} = 1\text{ mA}$$

$$I_3 = I_1 + I_2 = 3\text{ mA}$$

$$V_3 = (3\text{ k}\Omega) I_3 = 9\text{ V}$$

$$V_4 = V_3 + V_2 = 25\text{ V}$$

$$\frac{V_o}{75\text{ V}} = \frac{4\text{ V}}{25\text{ V}} \Rightarrow V_o = 12\text{ V}$$