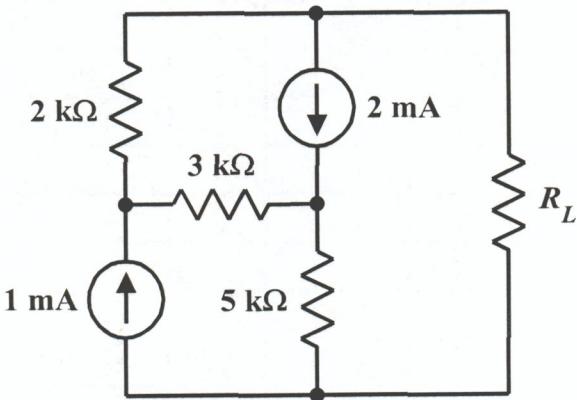


EE 2240  
Problem #02


- a. Find the value of  $R_L$  for maximum power transfer.



$\text{Req} = 2\text{k}\Omega + 3\text{k}\Omega + 5\text{k}\Omega = 10\text{k}\Omega$

$\therefore \text{Choose } R_L = 10\text{k}\Omega \text{ for maximum power transfer}$

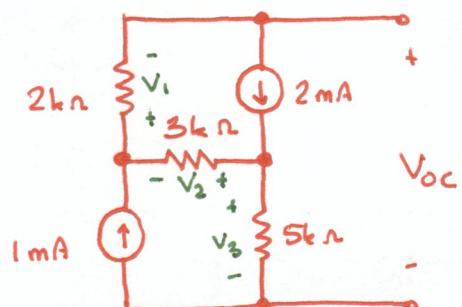- b. What is the maximum power that can be transferred?



$$V_1 = (2\text{k}\Omega)(2\text{mA}) = 4\text{V}$$

$$V_2 = (3\text{k}\Omega)(2\text{mA} - 1\text{mA}) = 3\text{V}$$

$$V_3 = (5\text{k}\Omega)(1\text{mA}) = 5\text{V}$$

$$V_{oc} = -V_1 - V_2 + V_3 = -4\text{V} - 3\text{V} + 5\text{V} = -2\text{V}$$

$$P_{max.} = \frac{\left(\frac{1}{2}V_T\right)^2}{R_L} = \frac{\left(\frac{1}{2}V_{oc}\right)^2}{R_L} = \frac{\left(\frac{1}{2}V_{oc}\right)^2}{10\text{k}\Omega} = \frac{(1\text{V})^2}{10\text{k}\Omega} = 100\mu\text{W}$$