

EE 2240
Problem #11

Use mesh analysis to find I_o .

