

EE 2240
Problem #01

Use the nodal analysis method to determine the value of V_x .

