

EE 2240
Problem #04

Use the nodal analysis method to determine the voltage, V_x , across the 4-siemens conductance.

