

EE 2240  
**Problem #05**

Use the nodal analysis method to determine the voltage across the  $10\ \Omega$  resistor. Then apply Ohm's Law to determine  $I$ .

