

EE 2240
Problem #06

Use the nodal analysis method to determine V_x .

