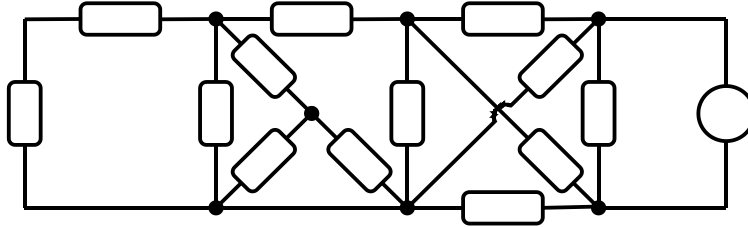


EE 2240
Problem #05



- How many nodes does the circuit have?
- How many branches does the circuit have?