

EE 2240  
**Problem #02**

Use Norton's theorem to find  $I_o$ .

