

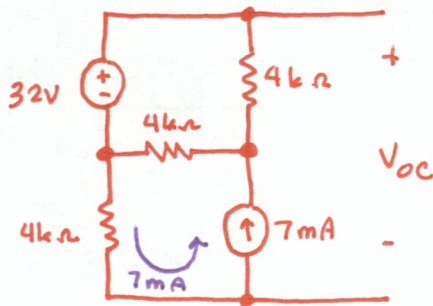


EE 2240
Problem #03

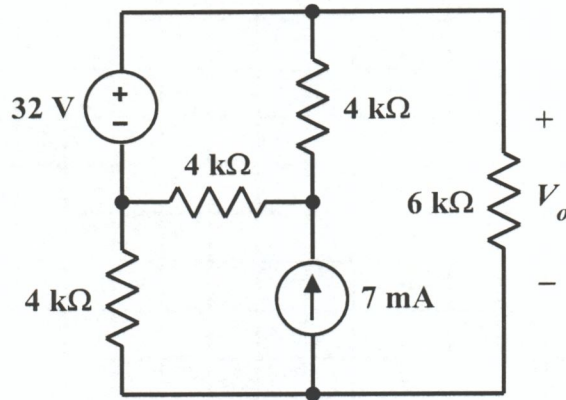The $6\text{k}\Omega$ resistor is the load for this circuit. Use the method described in class to find the Norton equivalent of the remainder of the circuit. (*Why not use source transformations?*) Then determine the value of V_o .


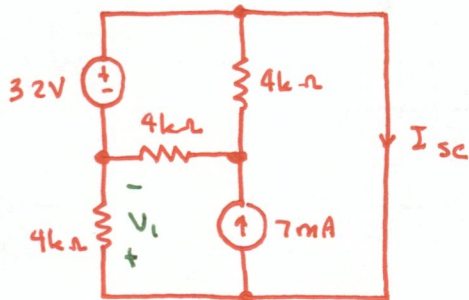
$$V_{oc} = 32\text{V} + (4\text{k}\Omega)(7\text{mA}) = 60\text{V}$$




$$V_1 = 32\text{V}$$

$$\begin{aligned} I_{sc} &= 7\text{mA} + \frac{V_1}{4\text{k}\Omega} \\ &= 7\text{mA} + \frac{32\text{V}}{4\text{k}\Omega} \\ &= 15\text{mA} \end{aligned}$$

$$I_N = I_{sc} = 15\text{mA}$$
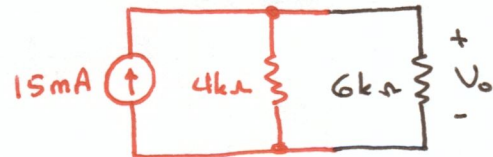
$$R_N = \frac{V_{oc}}{I_{sc}} = \frac{60\text{V}}{15\text{mA}} = 4\text{k}\Omega$$



$$\begin{aligned} V_o &= (15\text{mA}) \left(\frac{4\text{k}\Omega \cdot 6\text{k}\Omega}{4\text{k}\Omega + 6\text{k}\Omega} \right) \\ &= 36\text{V} \end{aligned}$$