

EE 2240  
**Problem #03**

If the  $10\text{ k}\Omega$  resistor absorbs  $2.5\text{ mW}$ , find  $V_s$ .

