

EE 2240
Problem #04

The power absorbed by R_x is 5 mW. Find R_x .

