

EE 2240
Problem #01

Find V_o .

