

EE 2240
Problem #02

Assume the op amp is ideal, and find V_o .

