

EE 2240
Problem #03

Find V_o in the network shown.

