

EE 2240
Problem #04

Assume the op amp is ideal, and find V_o .

