

EE 2240
Problem #05

What value of R is required so that 10 mW is delivered to the 10 k Ω resistor?

