

EE 2240  
Problem #09

Determine the output voltage  $V_o$  of the op-amp circuit shown.

