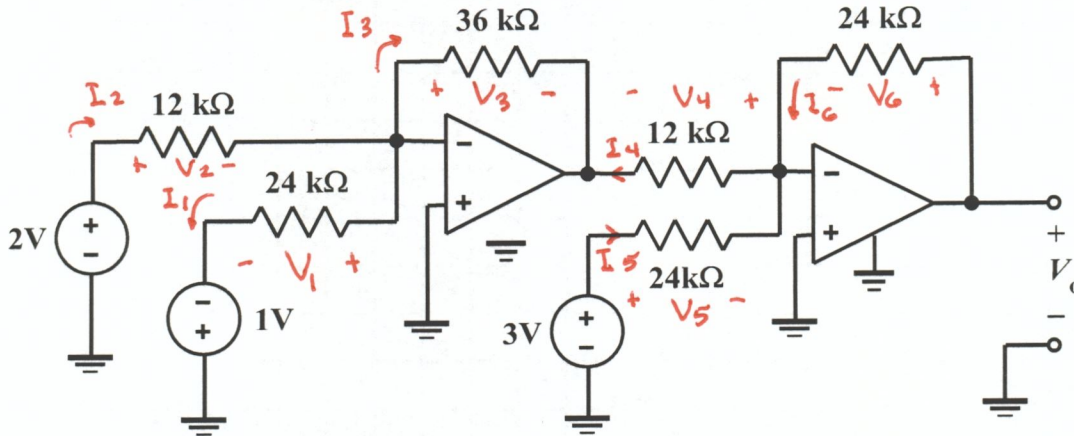


EE 2240
Problem #09

Determine the output voltage V_o of the op-amp circuit shown.



$$V_1 = 1V \Rightarrow I_1 = \frac{V_1}{24k\Omega} = \frac{1}{24} \text{ mA}$$

$$V_2 = 2V \Rightarrow I_2 = \frac{V_2}{12k\Omega} = \frac{1}{6} \text{ mA}$$

$$I_3 = I_2 - I_1 = \frac{1}{6} \text{ mA} - \frac{1}{24} \text{ mA} = \frac{1}{8} \text{ mA}$$

$$V_3 = (36k\Omega) I_3 = (36k\Omega) \left(\frac{1}{8} \text{ mA}\right) = 4.5V$$

$$V_4 = V_3$$

$$I_4 = \frac{V_4}{12k\Omega} = \frac{4.5V}{12k\Omega} = \frac{3}{8} \text{ mA}$$

$$V_5 = 3V$$

$$I_5 = \frac{V_5}{24k\Omega} = \frac{3V}{24k\Omega} = \frac{1}{8} \text{ mA}$$

$$I_6 = I_4 - I_5 = \frac{3}{8} \text{ mA} - \frac{1}{8} \text{ mA} = \frac{1}{4} \text{ mA}$$

$$V_6 = (24k\Omega) I_6 = (24k\Omega) \left(\frac{1}{4} \text{ mA}\right) = 6V$$