

EE 2240
Problem #06

Determine whether each component *absorbs* or *delivers* power. In each case, also calculate how much power is absorbed or delivered.

