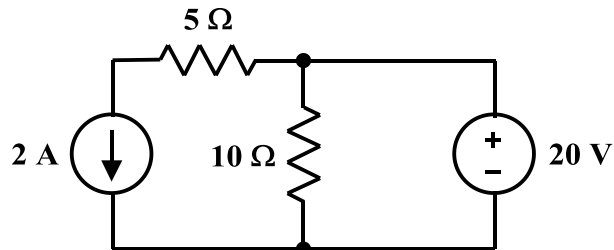


EE 2240
Problem #10

Given the circuit shown below:



- How much power does the 5Ω resistor absorb?
- How much power does the 10Ω resistor absorb?
- Does the independent current source deliver power or absorb power? How much?
- Does the independent voltage source deliver power or absorb power? How much?