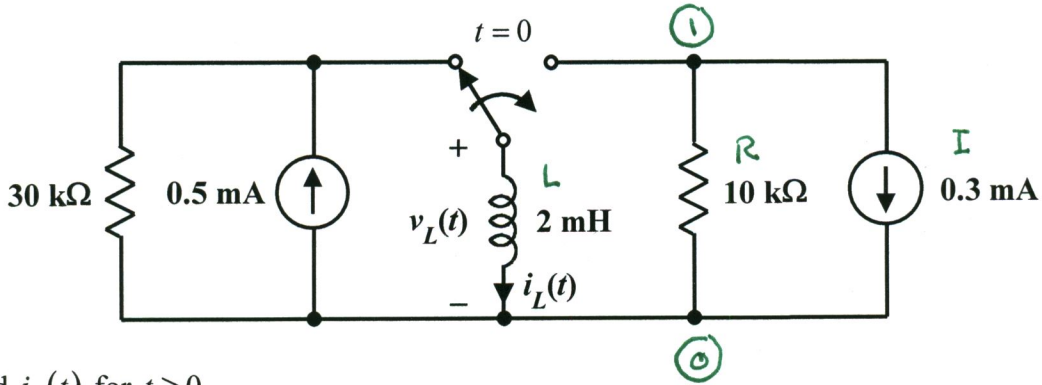


EE 2240
Problem #04

The switch has been in the position shown for a *very* long time.



a. Find $i_L(t)$ for $t \geq 0$.

$$i_L(0) = 0.5 \text{ mA}$$

$$\tau = \frac{2 \text{ mH}}{10 \text{ k}\Omega} = 200 \text{ ns}$$

$$i_L(\infty) = -0.3 \text{ mA}$$

$$\begin{aligned} i_L(t) &= [i_L(0) - i_L(\infty)] e^{-t/\tau} + i_L(\infty) \\ &= [0.5 - (-0.3)] e^{-t/200 \times 10^{-9}} + (-0.3) \text{ mA} \\ &= 0.8 e^{-5 \times 10^6 t} - 0.3 \text{ mA}, \quad t \geq 0 \end{aligned}$$

b. Use PSpice and PROBE to plot the power delivered by the 0.3 mA independent current source for $0 \leq t \leq 1 \mu\text{s}$.

Problem #04

L 1 0 2m IC=0.5m

R 1 0 10k

I 1 0 DC 0.3m

.TRAN 1n 1u 0 1n UIC


.PROBE

.END

5e = 1μs

See the next page for the plot.

Problem #04

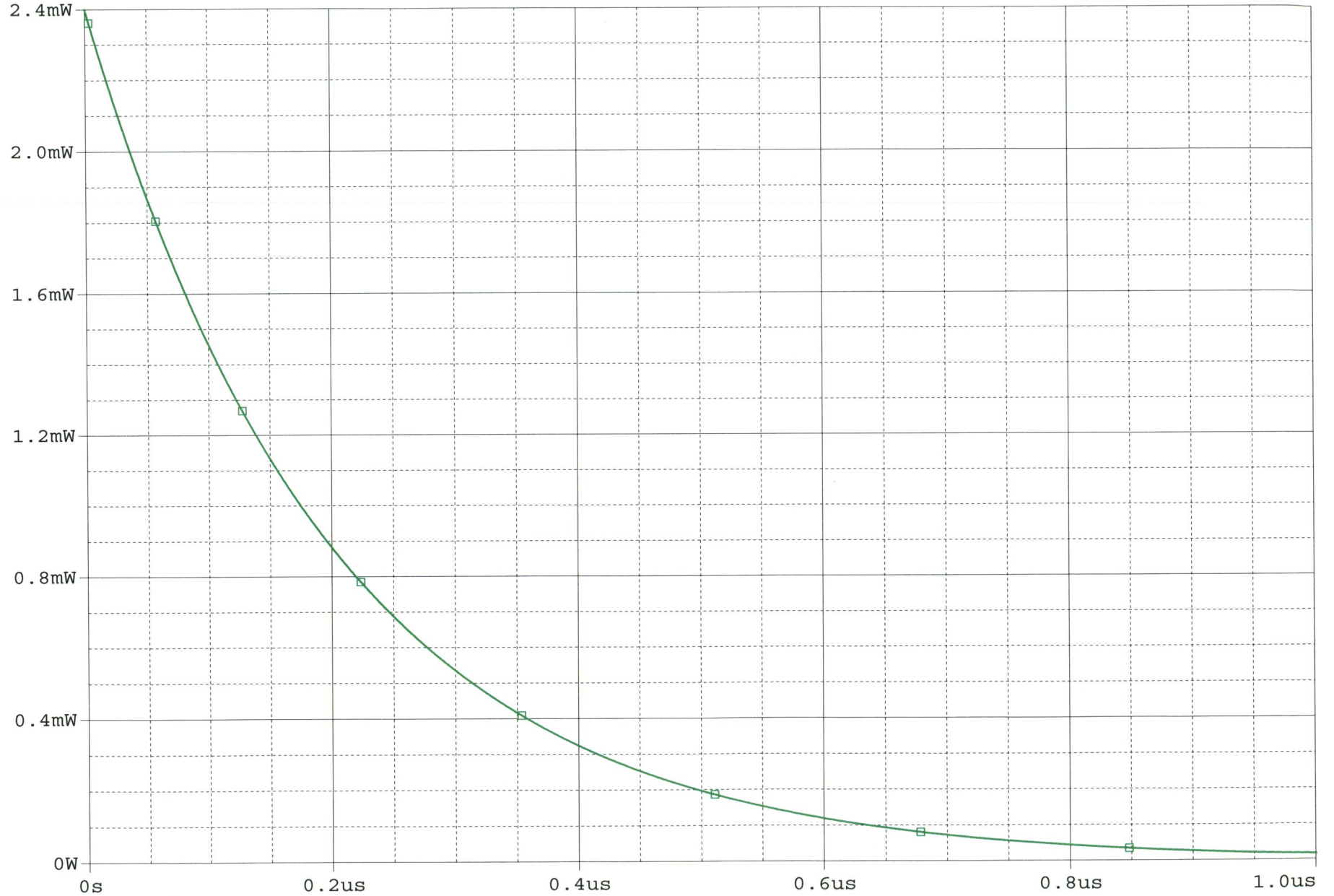

□ $-W(I)$ ← Note: $W(I)$ is power absorbed, $-W(I)$ is power delivered. Time