

EE 2240
Problem #05

The circuit has reached the DC steady state prior to $t = 0$. Find $i(t)$ for $t \geq 0$.

