

EE 2240
Problem #08

Find $i(t)$ for $t \geq 0$ in the circuit shown and accurately sketch a plot of the response including a brief time interval just prior to switch movement.

