

EE 2240
Problem #01

For the underdamped circuit shown, determine the voltage $v(t)$ if the initial conditions on the storage elements are $i_L(0) = 1$ A and $v_C(0) = 10$ V.

