

EE 2240
Problem #04

Find $v_C(t)$ for $t > 0$ if $v_C(0) = 0$ V and $i_L(0) = 0$.

